

1. In the circuit shown,  $A$  and  $B$  are the inputs and  $F$  is the output. What is the functionality of the circuit?  
(GATE-EC2019,15)

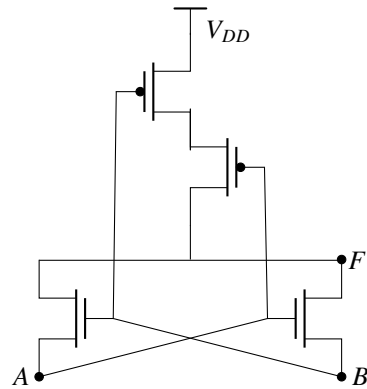


Figure 1: Circuit Diagram

1. Latch
2. XNOR
3. SRAM Cell
4. XOR